

classical computing


Lecture 1

By Maria Delgado


History of classical computing

• WHAT IS COMPUTATION

 - A mathematical calculation that maps inputs to an output based on a set of instructions.



• BIT-SIZED HISTORY OF COMPUTING

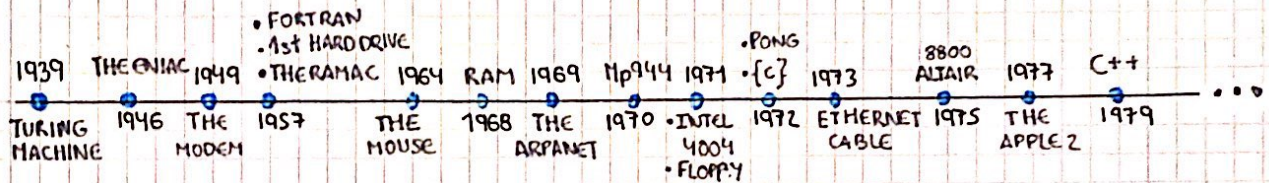

Base-representations

"Learning to think like a computer"

* Decimals

- Decimal number system is based on numerical digits 0-9
- Base determines how numbers get represented and how we perform arithmetic operations

Ex: $6 = 6$

$$= (6 \cdot 10^0)$$

$36 = 30 + 6$

$$= (3 \cdot 10^1) + (6 \cdot 10^0)$$

$536 = 500 + 30 + 6$

$$= (5 \cdot 10^2) + (3 \cdot 10^1) + (6 \cdot 10^0)$$

* Binary

- We can describe any number with BITS
- Base-2 is one of the most important bases for performing computation
- It is Binary, only 0 and 1
- Also referred to as a BIT
- We can still do operations, all of the operations in a classical computer happen by manipulating BITS

CONVERTING

$1010 \rightarrow \text{decimal}$

$$= (1 \cdot 10^3) + (0 \cdot 10^2) + (1 \cdot 10^1) + (0 \cdot 10^0)$$

$1010 \rightarrow \text{binary}$

$$= (1 \cdot 2^3) + (0 \cdot 2^2) + (1 \cdot 2^1) + (0 \cdot 2^0) = 8 + 2 = 10$$

Base $\left\{ \begin{array}{l} \text{Binary: } 2^0 \approx 11 = 1 \cdot 2^1 + 1 \cdot 2^0 = 3 \\ \text{Decimal: } 10^0 \approx 11 = 1 \cdot 10^1 + 1 \cdot 10^0 \end{array} \right.$

BITS: arithmetic operators

"How computers compute"

* BINARY ADDITION

- Similar to the decimal we are used to
- BITS carry over when the sum becomes larger than 2

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10$$

* MULTIPLYING BITS

- BINARY MULTIPLICATION
- It's like 'normal' one (like the decimal)

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$


$$1 \cdot 1 = 1$$

Why BITS


- Easier for Building Hardware
- Fast Operations

Boolean Logic

 
• Boolean logic: Maps Input bit(s) to output bit(s)



AND
Both

 

OR
Either Term

 

NOT
Just 1 Term

• Logic gates + Truth Tables

• Logic: Maps Input bit(s) to output bit(s)

• Truth Tables: Tells us the output of a logical operation based on its input

Gates 1 BIT

• Gates: NOT


• Not: flips the bit



INPUT	OUTPUT
0	1
1	0

• Gates: FANOUT

• Fanout: copies the bit

 

a	OUTPUT
0	00
1	11

Gates 2BIT

• Gates: AND

- outputs 1 if both are 1, outputs 0 otherw.



a	b	OUTPUT
0	0	0
0	1	0
1	0	0
1	1	1

• Gates: OR

- outputs 1 if either of the input bits is 1 outputs 0 if neither of the inputs bits is 1



a	b	OUTPUT
0	0	0
0	1	1
1	0	1
1	1	1

• Gates: XOR

- Outputs 1 if either input bits are 1, but not both outputs 0 if neither or both bits are 1



a	b	OUTPUT
0	0	0
0	1	1
1	0	1
1	1	0


$a \oplus b$

$a \otimes b$

universality

- Any computation operation can be made by using a combination of {NOT, AND, OR, FANOUT}

~Gates: NAND \rightarrow (NOT + AND)

 

a	b	c
0	0	0
0	1	0
1	0	0
1	1	1

c	OUT
0	1
1	0

a	b	OUT
0	0	1
0	1	1
1	0	1
1	1	0

"Let's make a Binary adder with the gates we have" $a + b =$

a	b	OUT ₁	OUT ₂
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

a	b	Bit ₀
0	0	0
0	1	1
1	0	1
1	1	0


OUT₂ \rightarrow

a	b	Bit ₁
0	0	0
0	1	0
1	0	0
1	1	1

OUT₁ \rightarrow

OUT₂ \rightarrow XOR \rightarrow

OUT₁ \rightarrow AND \rightarrow

 

Reversibility

- Given the output of a gate, we can determine what the inputs are

• Is NOT reversible?

YES

output 1 \rightarrow 0

output 0 \rightarrow 1

• Is AND reversible?

NO

output 1 \rightarrow 1, 1

output 0 \rightarrow 0, 0
 \rightarrow 0, 1
 \rightarrow 1, 0

\rightarrow REVERSIBLE GATE: preserves all the information

\rightarrow NON-REVERSIBLE GATE: loses some information